
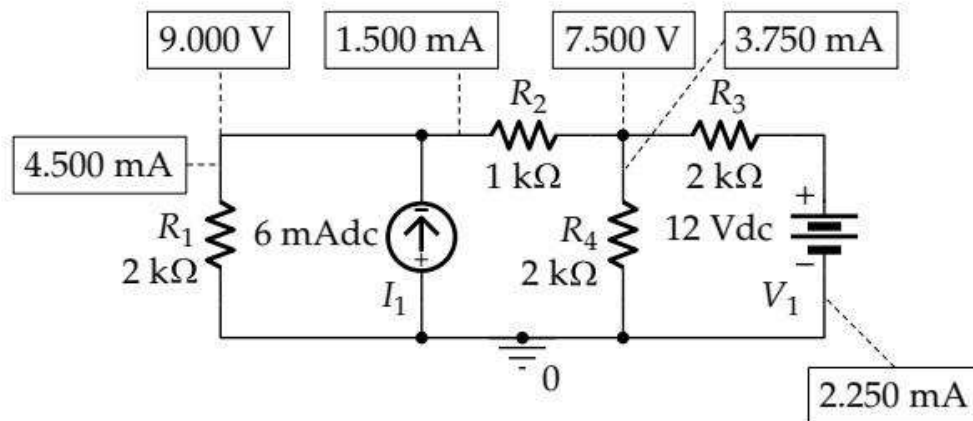


Getting started with Xschem with NGSPICE

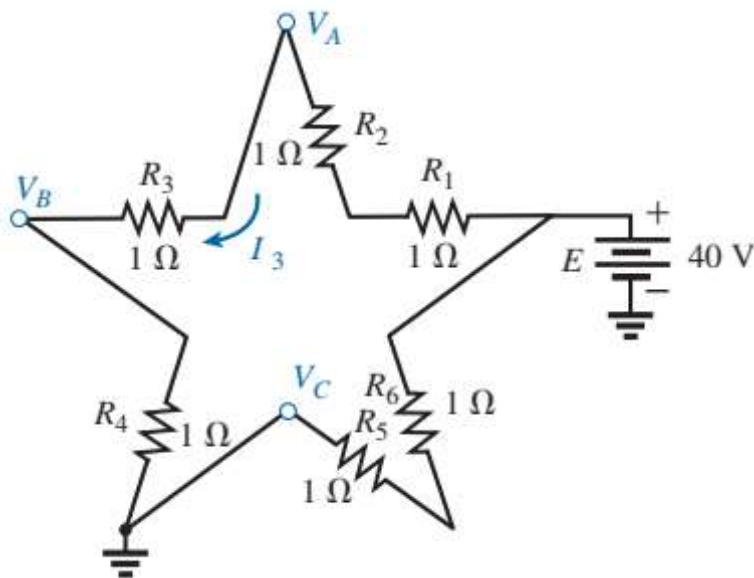Verify the following circuit using Xschem and write netlist verify the results



- Find the voltage V_C .
- Determine the voltage V_A .
- Find the voltage V_B .
- Calculate the current I_3



Answers : $V_C=0$, $V_A=20$ V . $V_B=10$ V, $I_3=10$ Amp