 



# Design Rules

**Pravin Zode**


# Minimum Size Transistor




# Minimum Size NMOS and PMOS

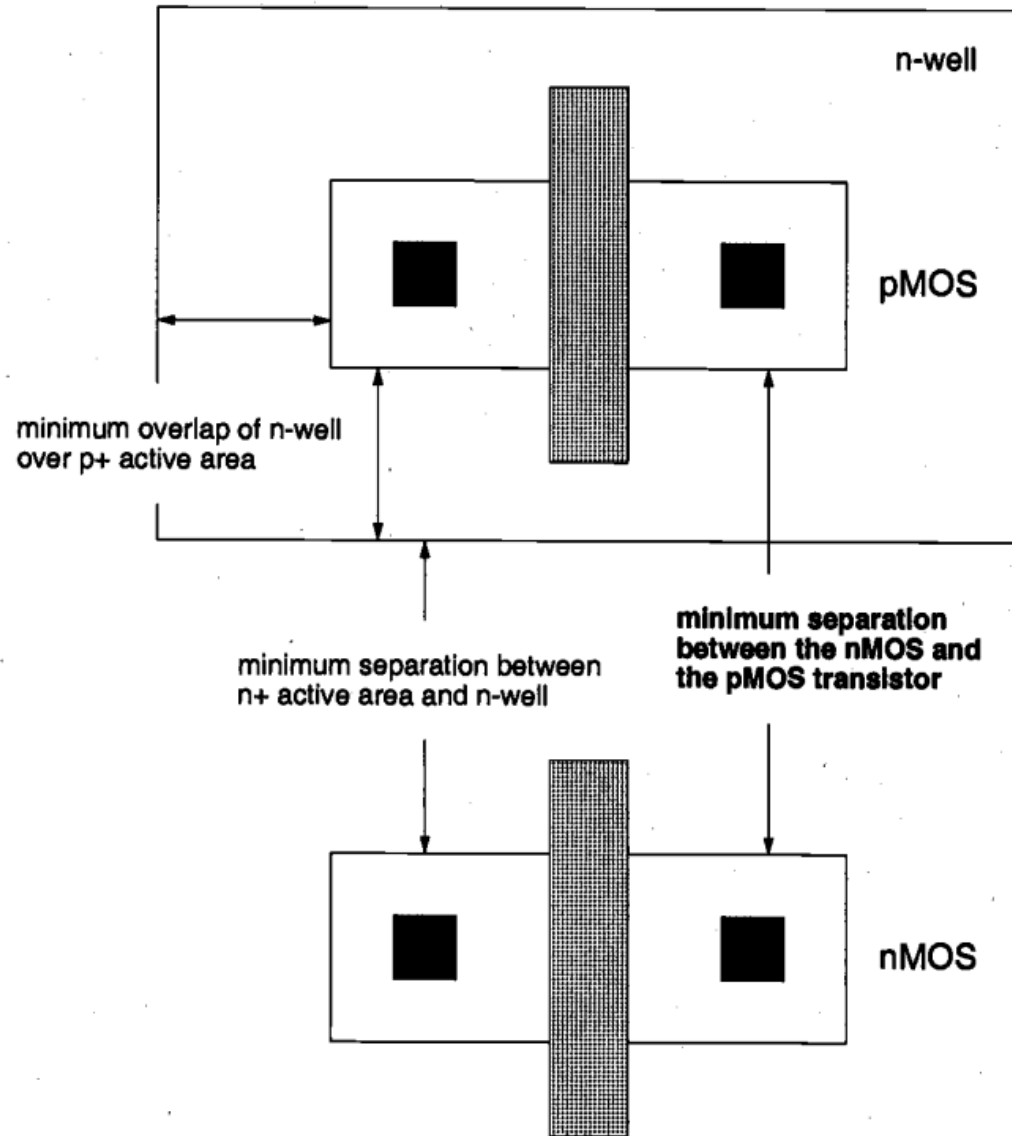


# Cross Section and Layout

 

(a) Layout

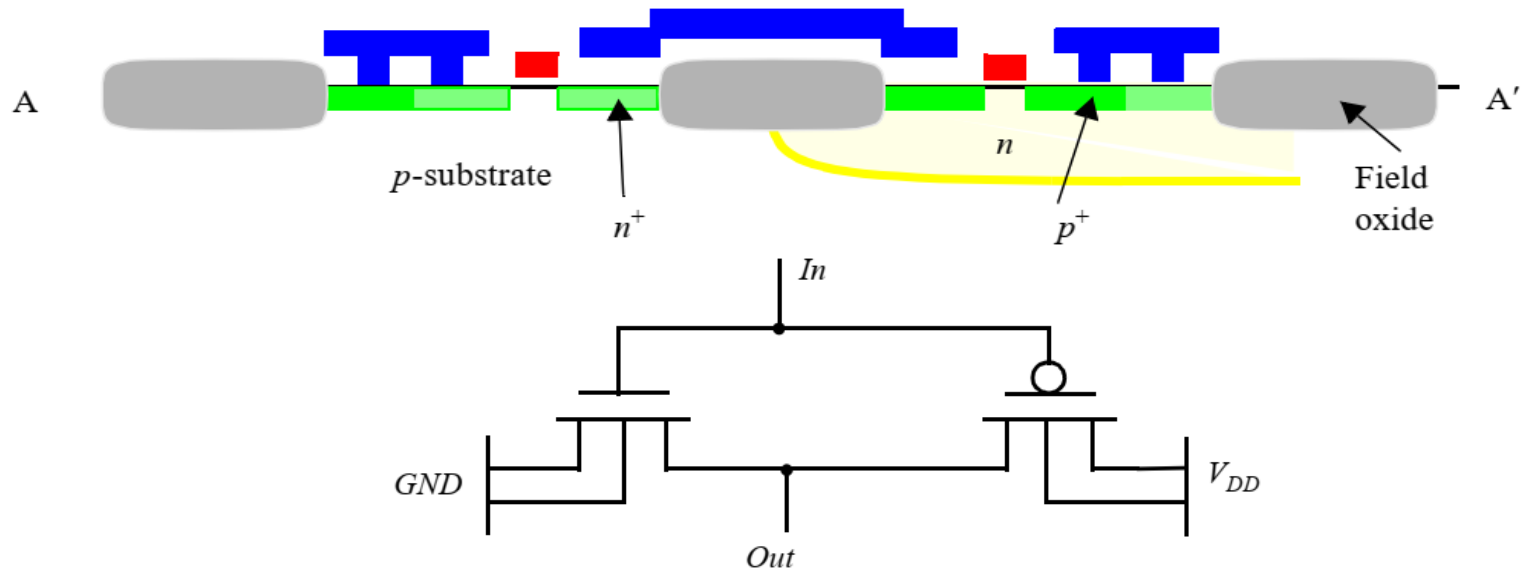

# Inverter Layout

 

## Inverter Layout

**NOT to scale!**

 


Fig: 1


 


Fig: 2

# Inverter Layout

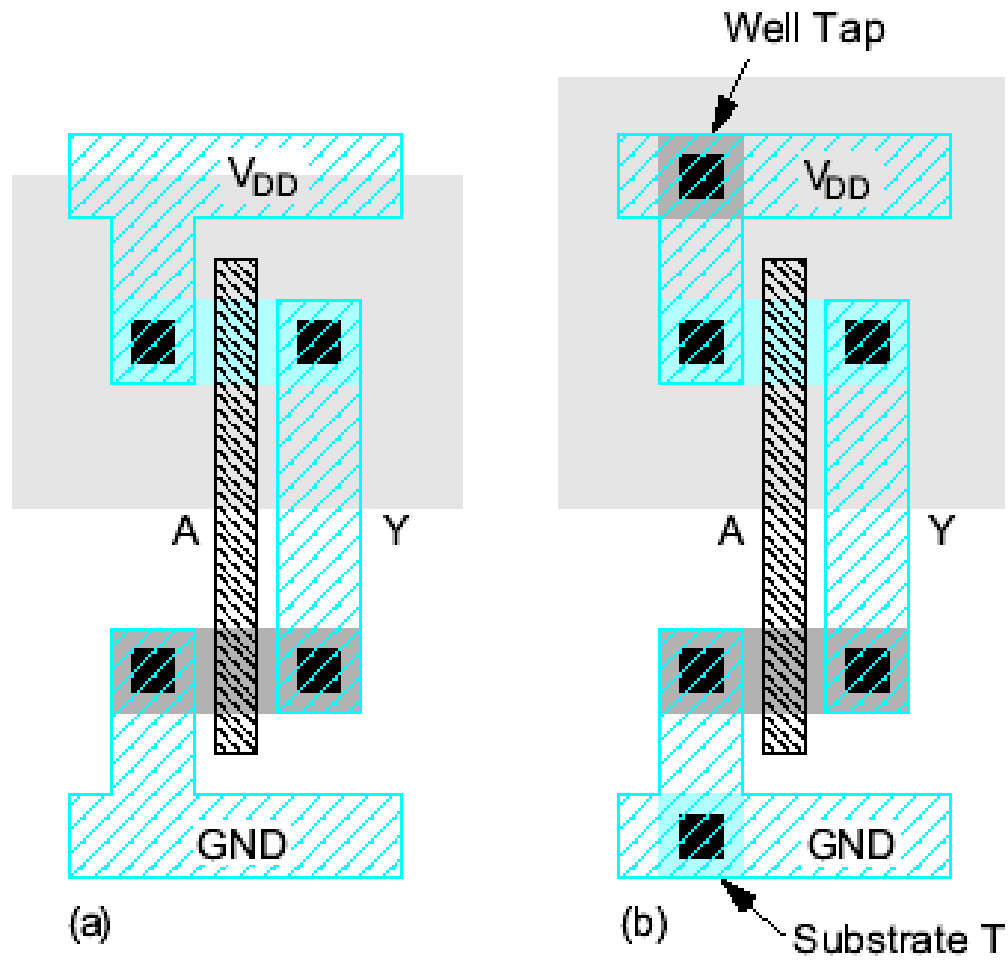

# NAND Gate Layout

## NAND Gate Layouts

 
 


FIG :3


 



FIG :4

# Example

 





# Simplified Lambda Rules

 


# Spacing between NMOS & PMOS

 

# Spacing between NMOS & PMOS

 


# 3-Input NAND Gate Layout

 


# Compound Gate Layout

Example : O3AI Sketch a stick diagram for O3AI and estimate area

$$Y = \overline{(A + B + C)} \cdot D$$

 

 

**Thank you !**

**Happy Learning**