


The Inverter

Pravin Zode

Outline



- Inverter Basics
- Transient Response
- DC Characteristics
- Beta Ratio Effect
- Noise Margin

Inverter Basics

 


- PMOS on top (connected to V_{DD})
- NMOS on bottom (connected to GND)
- Both gates connected to input V_{in}
- Drains connected together to form output V_{out}

Inverter DC Analysis

  


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

Inverter Transient Response


 


(a) Low-to-high

 


(b) High-to-low


CMOS Inverter Load Characteristics

  

Inverter DC Characteristics

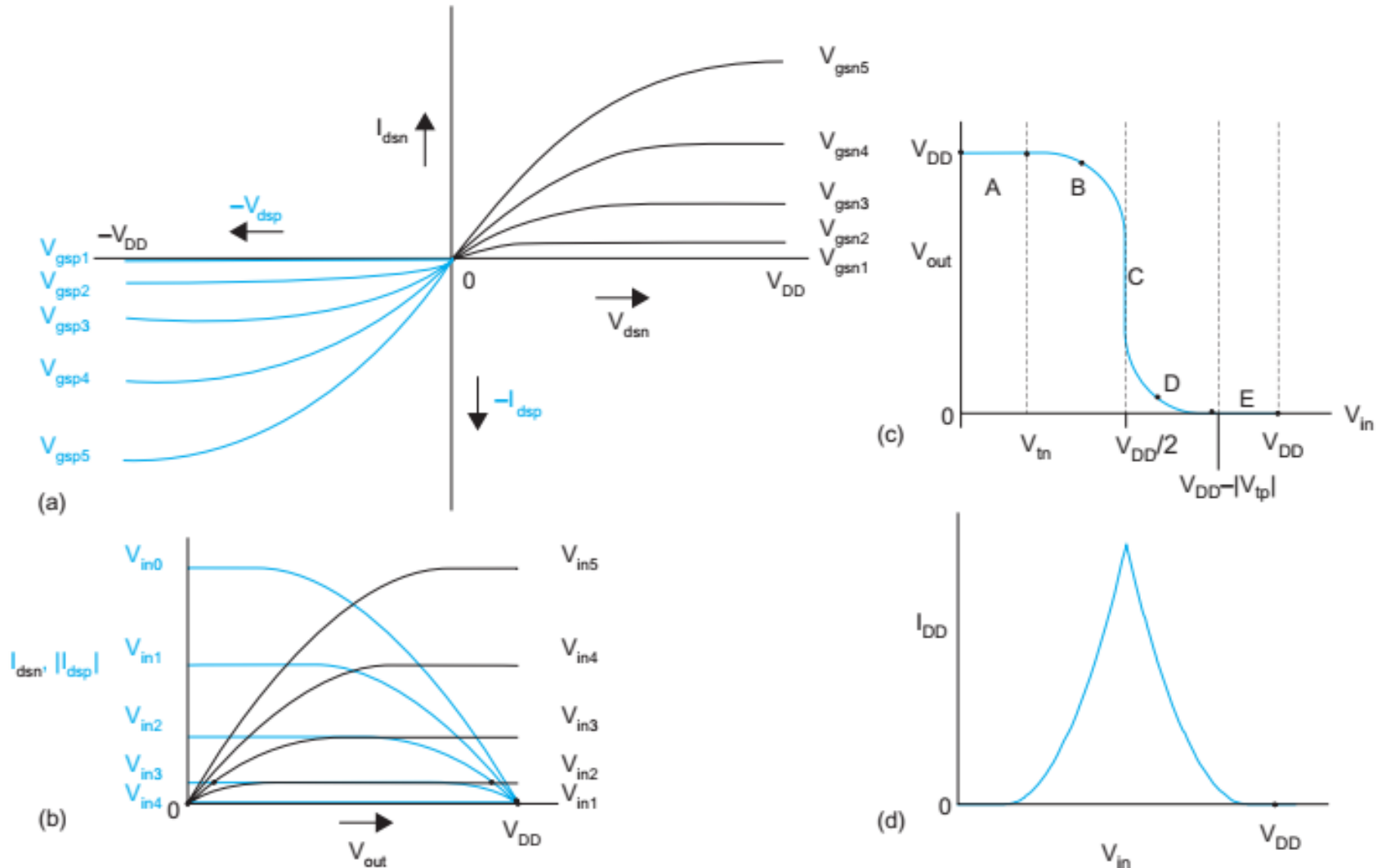

Inverter DC Characteristics

 


Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

Inverter Threshold

- Inverter threshold is the input voltage at which the output voltage = input voltage for an inverter
- **Ideal condition: $V_{dd} / 2$**
- Why it is desirable
 - Maximum noise margin
 - Equal rise and fall times for charging/discharging capacitive loads
 - Balanced PMOS (pull-up) and NMOS (pull-down) strengths

Beta Ratio Effect

 

- Inverters with different beta ratios $r = \beta_p / \beta_n$ are called skewed inverters
 - $r > 1$: **HI-skewed** – stronger pMOS → higher threshold
 - $r < 1$: **LO-skewed** – weaker pMOS → lower threshold
 - $r = 1$: **Unskewed** inverter – balanced


Impact of Skewing:

- Alters switching threshold in DC transfer characteristics
- Sharp transitions maintained despite skewing

Noise Margin

- Noise margin quantifies the tolerance to unwanted voltage fluctuations (noise) on the input without corrupting the output
- Closely related to the DC voltage transfer characteristics
- Characterized by two parameters:
 - LOW Noise Margin (NML) → Tolerance for noise in logic '0' region
 - HIGH Noise Margin (NMH) → Tolerance for noise in logic '1' region

Noise Margin

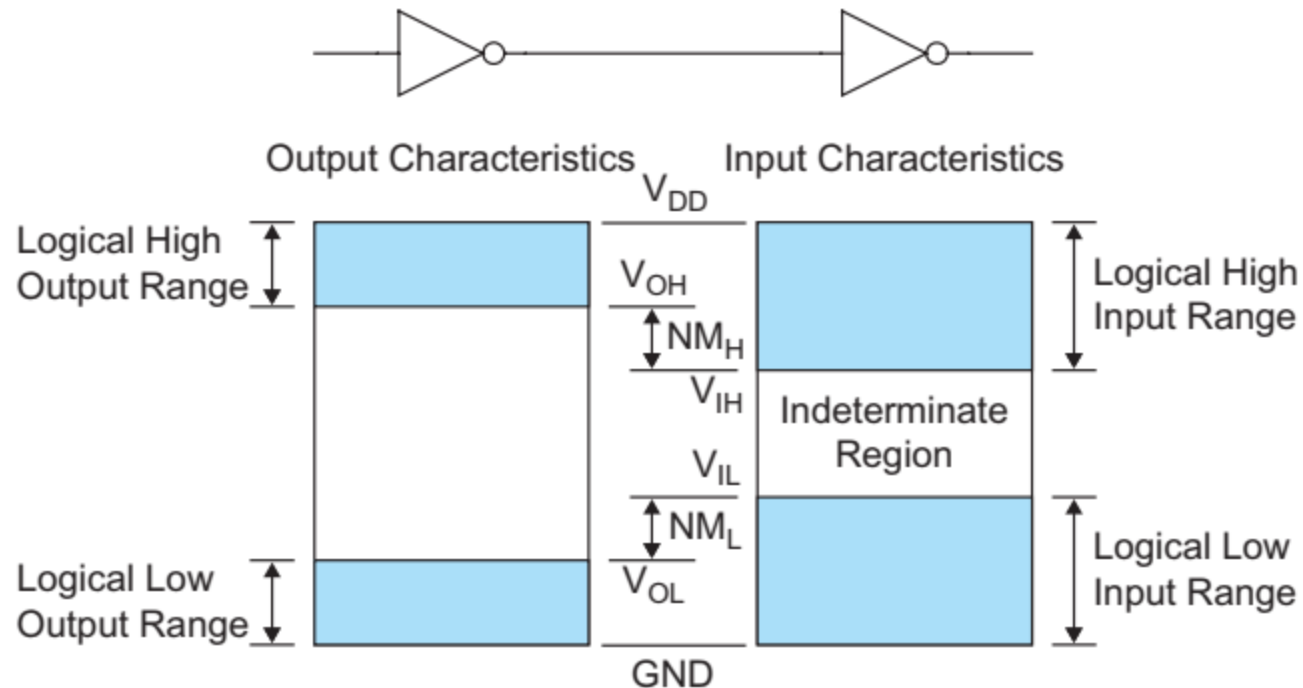

where

V_{IH} = minimum HIGH input voltage
 V_{IL} = maximum LOW input voltage
 V_{OH} = minimum HIGH output voltage
 V_{OL} = maximum LOW output voltage


$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

Noise Margin

- Let's say a gate outputs a logical HIGH as $V_{OH} = 4.8V$, and the next gate requires at least $V_{IH} = 3.5V$ to reliably detect a HIGH:
 $NMH = V_{OH} - V_{IH} = 4.8V - 3.5V = 1.3V$
- This means: Up to 1.3V of noise can interfere, and the signal will still be understood as HIGH
- Similarly, for LOW:
- Suppose $V_{OL} = 0.2V$, and the input accepts LOWs up to $V_{IL} = 1V$:
 $NML = V_{IL} - V_{OL} = 1V - 0.2V = 0.8V$
- So, up to 0.8V of noise can be tolerated while still being recognized as LOW.

Inverter Noise Margin

 

- If NML or NMH is small, gate is more susceptible to input noise
- Unskewed gates have balanced noise margins, improving resistance to random noise
- Skewed gates can favor NMH or NML depending on the dominant input noise condition
- Speed vs. noise margin is a common trade-off; higher speed often reduces noise margins
- Noise margins are relative to V_{DD} , 0.4 V margin is good in 1.8 V process but poor in 5 V.

Summary

- Beta ratio determines the inverter's switching threshold
 - $r = 1 \rightarrow$ Balanced inverter $\rightarrow V_{DD} / 2$
 - $r > 1 \rightarrow$ HI-skewed (stronger pMOS) \rightarrow Higher threshold
 - $r < 1 \rightarrow$ LO-skewed (stronger nMOS) \rightarrow Lower threshold
- Skewing affects rise/fall times, noise margins, and power
- Adjusted by changing transistor widths
- Noise Margin defines tolerance to unwanted input voltage noise
- Larger noise margins \rightarrow More reliable operation
- Unity gain point (slope = -1) defines logic levels
- Expressed relative to V_{DD} for process scaling



Thank you !

Happy Learning