

# SPICE

**Pravin Zode**

# Outline

- Introduction to Design
- Types of Analysis
- Scale factors
- Element Conventions
- Circuit Descriptions
- Examples

# Introduction

- SPICE (Simulation Program with Integrated Circuit Emphasis)
- It is powerful circuit simulation tool that allows engineers to analyze and design electronic circuits with great accuracy
- SPICE allows for the creation of accurate circuit models to simulate real-world behavior
- Accurate prediction of circuit behavior without physical prototypes
- SPICE can perform a variety of analyses, including DC, AC, transient, and more
- Saves time and cost by detecting issues early in the design process.

# Types of Analysis

- **DC Analysis** : SPICE can determine the steady-state behavior of analog circuits, such as bias points and power consumption
- **AC Analysis** : SPICE can simulate the frequency response of analog circuits, including gain, phase, and bandwidth
- **Transient Analysis** : SPICE can model the dynamic behavior of analog circuits, including response to step inputs and oscillations

# Digital Circuit Simulation

- SPICE can accurately simulate the behavior of digital logic gates, including propagation delays and logic levels
- SPICE can model the behavior of flip-flops, registers, and other sequential logic circuits
- SPICE can perform timing analysis on digital circuits, ensuring proper operation and identifying potential timing issues

# Advanced Simulation Features

- **Monte Carlo Analysis** : SPICE can perform statistical analysis to assess the impact of component variations on circuit performance
- **Parametric Sweeps** : SPICE allows for the simulation of circuits with varying parameter values, enabling design optimization
- **Optimization Algorithms** : SPICE can be coupled with optimization algorithms to automate the design process

# Scale Factors

| Suffix | Name  | Factor                |
|--------|-------|-----------------------|
| T      | Tera  | $10^{12}$             |
| G      | Giga  | $10^9$                |
| Meg    | Mega  | $10^6$                |
| K      | Kilo  | $10^3$                |
| mil    | Mil   | $25.4 \times 10^{-6}$ |
| m      | milli | $10^{-3}$             |
| u      | micro | $10^{-6}$             |
| n      | nano  | $10^{-9}$             |
| p      | pico  | $10^{-12}$            |
| f      | femto | $10^{-15}$            |
| a      | atto  | $10^{-18}$            |

# Element Conventions

|   |  |
|---|--|
| A | XSPICE code model                            |
| B | Behavioral (arbitrary) source                |
| C | Capacitor                                    |
| D | Diode  |
| E | Voltage-controlled voltage source (VCVS)     |
| F | Current-controlled current source (CCCs)     |
| G | Voltage-controlled current source (VCCS)     |
| H | Current-controlled voltage source (CCVS)     |
| I | Current source                               |
| J | Junction field effect transistor (JFET)      |
| K | Coupled (Mutual) Inductors                   |
| L | Inductor                                     |
| M | Metal oxide field effect transistor (MOSFET) |

|   |  |
|---|--|
| N | Numerical device for GSS                             |
| O | Lossy transmission line                              |
| P | Coupled multiconductor line (CPL)                    |
| Q | Bipolar junction transistor (BJT)                    |
| R | Resistor   |
| S | Switch (voltage-controlled)                          |
| T | Lossless transmission line                           |
| U | Uniformly distributed RC line                        |
| U | Basic digital building blocks using XSPICE           |
| V | Voltage source                                       |
| W | Switch (current-controlled)                          |
| X | Subcircuit   |
| Y | Single lossy transmission line (TXL)                 |
| Z | Metal semiconductor field effect transistor (MESFET) |




# Circuit Description

- The first line in the input file must be the title, which is the only comment line that does not need any special character in the first place
- The last line must be .end, plus a newline delimiter
- Commands are specified by Dot Command ( .dc, .ac etc)
- Node "0" is always the ground (reference) node.
- Components are identified by letters based on their type, followed by numbers (e.g., R1, C1, M1)
- Comments are declared followed by ;
- A line may be continued by entering a '+' (plus) in column 1 of the following line

# Structure of SPICE Netlist

- Title
- Controls
- Sources
- Model
- Components
- Subcircuit


# Example-01 (Netlist)

 

```
Vin    1    0    DC    1
R1     1    2    1k
R2     2    0    2k
.end
```

```
v(1) = 1.000000e+00
v(2) = 6.666667e-01
vin#branch = -3.33333e-04
```


## Example-02 ( Node Name , op)

 

```
*#destroy all
*#run
*#print all
.op
Vin Vin 0 DC 1
R1 Vin Vout 1k
R2 Vout 0 2k
.end
```

```
v(1) = 1.000000e+00
v(2) = 6.666667e-01
vin#branch = -3.33333e-04
```

# Example-03 ( Transfer Function)

 


```
*#destroy all
*#run
*#print all
.op
Vin Vin 0 DC 1
R1 Vin Vout 1k
R2 Vout 0 2k
.end
```

```
.TF      V(Vout,0)      Vin
```

```
transfer_function = 6.666667e-01
output_impedance_at_v(vout,0) = 6.666667e+02
vin#input_impedance = 3.000000e+03
```

- "gain" of this voltage divider is  $2/3$
- Input resistance is  $3k = (1k + 2k)$
- Output resistance is  $667 = (1k || 2k)$

# Example-04 ( Transfer Function)

 


```
*#destroy all
*#run
*#print all
.op
Vin Vin 0 DC 1
R1 Vin Vout 1k
R2 Vout 0 2k
.end
```

```
.TF      V(Vout,0)      Vin
```

```
transfer_function = 6.666667e-01
output_impedance_at_v(vout,0) = 6.666667e+02
vin#input_impedance = 3.000000e+03
```

- "gain" of this voltage divider is  $2/3$
- Input resistance is  $3k = (1k + 2k)$
- Output resistance is  $667 = (1k || 2k)$


## Example-04 ( Transfer Function)

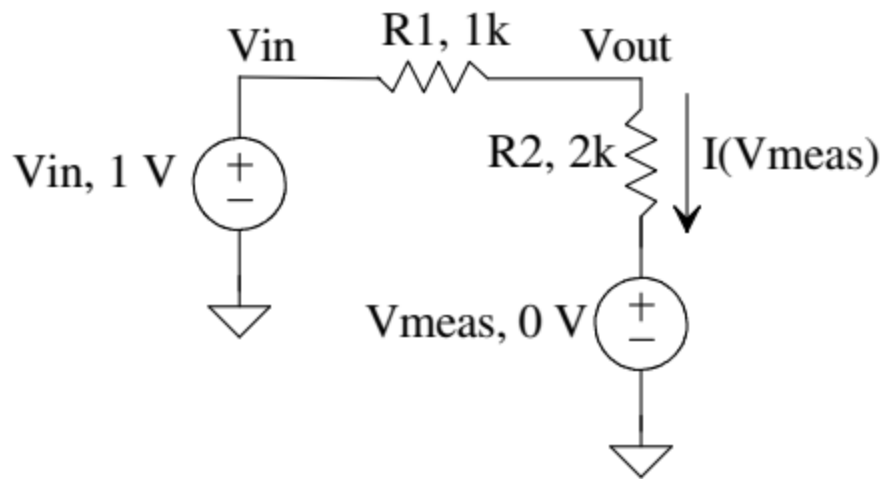

```
*#destroy all
*#run
*#print all
.TF I(Vmeas) Vin
Vin Vin 0 DC 1
R1 Vin Vout 1k
R2 Vout Vmeas 2k
Vmeas Vmeas 0 DC 0
.end
```

The gain is  $I(V_{meas})/V_{in}$  or  $1/3k$  ( $= 333 \mu\text{mhos}$ )

# Example-05 (VCVS)

 

```
.TF      V(Vout,0) Vin
Vin      Vin      0      DC      1
R1       Vb       0      3k
R2       Vt       Vout    1k
R3       Vout     0      2k
E1       Vt       Vb      Vin      0      23


.end
```

transfer\_function = 7.666667e+00  
output\_impedance\_at\_v(vout,0) = 1.333333e+03  
vin#input\_impedance = 1.000000e+20




 
# Example-06 ( Ideal OpAmp)



- Ideal op-amp can be implemented in SPICE with a VCVS or with a voltage controlled current source (VCCS)



 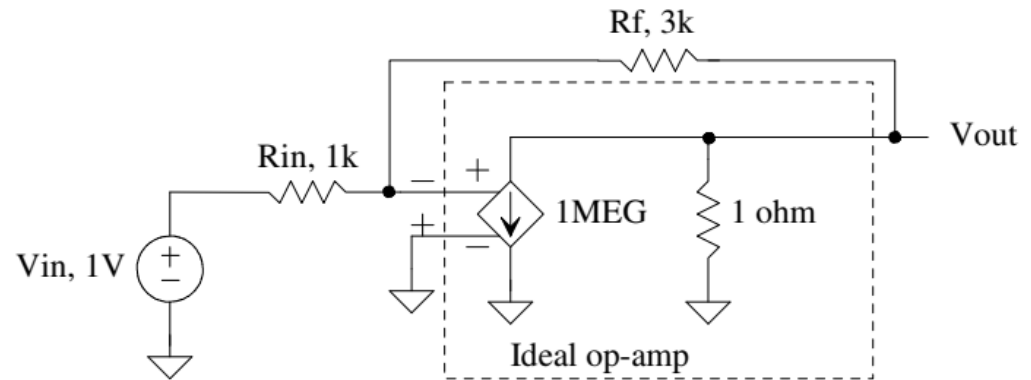Voltage-Controlled Current Source (VCCS)  
G1 n3 n4 n1 n2 G



# Example-07 ( Sub Circuit)

 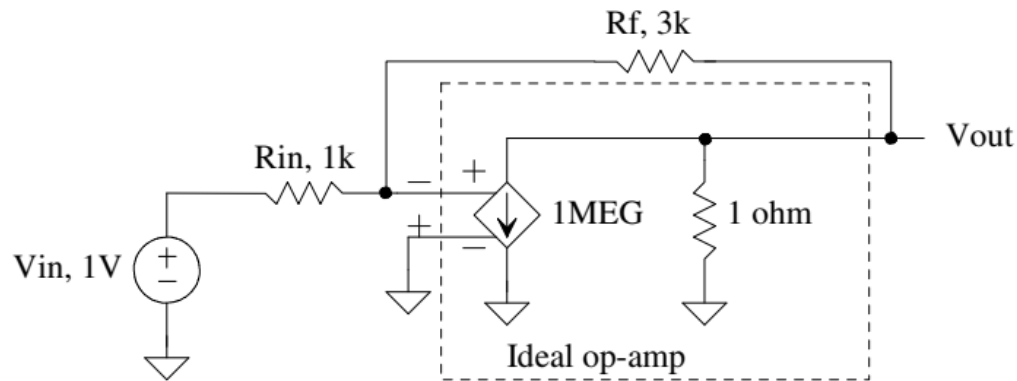

```

##destroy all
##run
##print all

```

```
.TF      V(Vout,0) Vin
```

```

Vin      Vin      0      DC      1
Rin      Vin      Vm      1k
Rf       Vout     Vm      3k

```

```
X1      Vout      0      vm      Ideal_op_amp
```

```

.subckt Ideal_op_amp Vout Vp Vm
G1      Vout      0      Vm      1MEG
RL      Vout      0      1
.ends
.end


```

```


transfer_function = -2.99999e+00
output_impedance_at_v(vout,0) = 3.999984e-06
vin#input_impedance = 1.000003e+03

```


# Example-08 ( DC Analysis )

 

 
```
*#destroy all
*#run
*#plot Vin Vout
.dc Vin 0 1 1m
Vin Vin 0 DC 1
R1 Vin Vout 1k
R2 Vout 0 2k
.end
```




# Example-09 ( Plotting IV Curve )

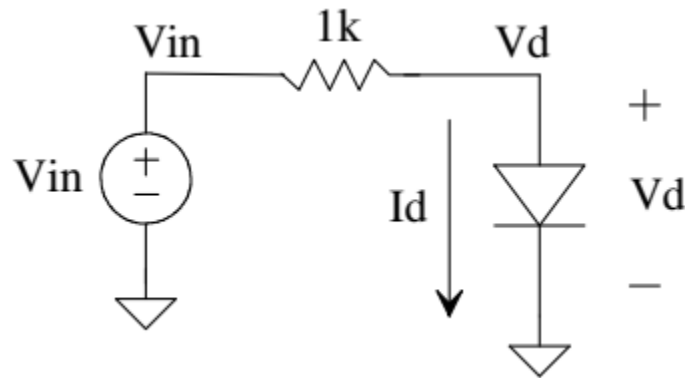

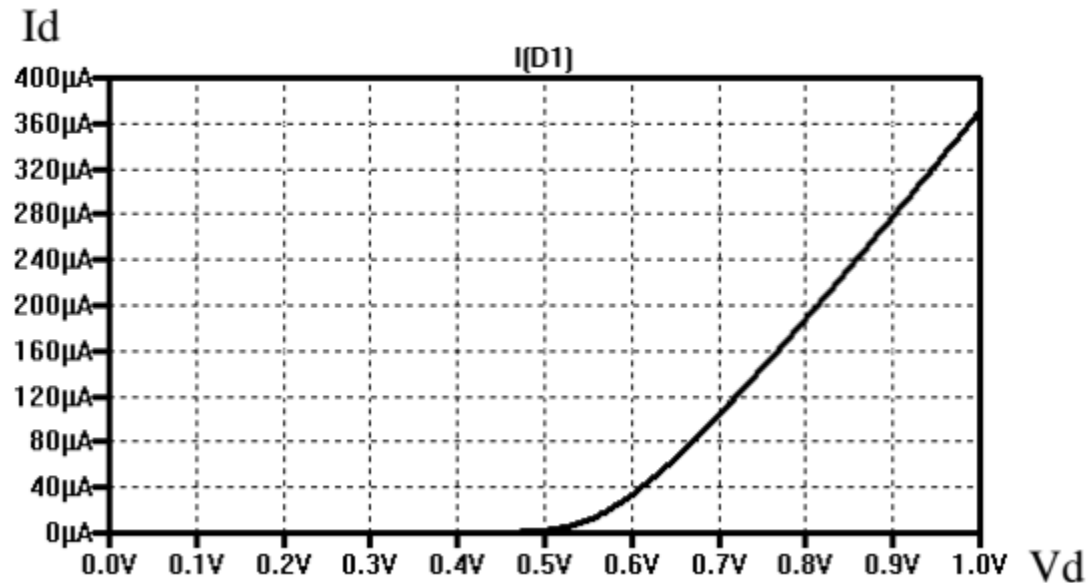
```
*#destroy all
*#run
*#let ID=-Vin#branch
*#plot ID
.dc Vin 0 1 1m
Vin Vin 0 DC 1
R1 Vin Vd 1k
D1 Vd 0 mydiode
.model mydiode D
end
```




# Example-09 ( DC Sweep )

 
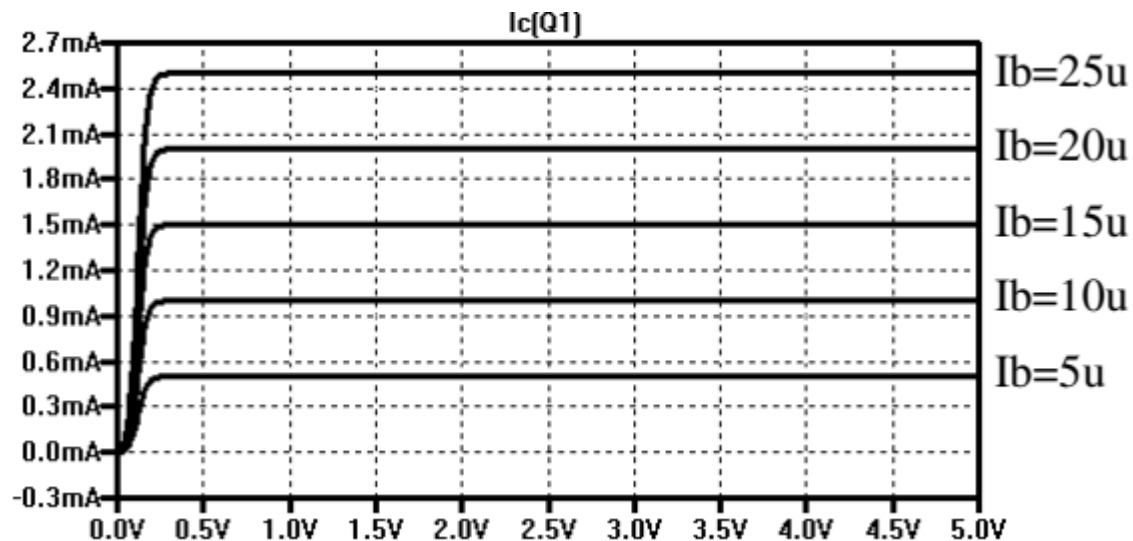
```
*#destroy all
*#run
*#let Ic=-Vce#branch
*#plot Ic
.dc Vce 0 5 1m Ib 5u 25u 5u
Vce Vce 0 DC 0
Ib 0 Vb DC 0
Q1 Vce Vb 0 myNPN
.model myNPN NPN
.end
```




# Example-10 ( Transient Analysis )

 


```
*#destroy all  
*#run  
*#plot vin vout
```

```
.tran 100p 100n
```

 
```
Vin      Vin      0      DC      1  
R1       Vin      Vout    1k  
R2       Vout     0      2k  
.end
```




# Example-11 ( Transient Analysis )

 

 
```
*#destroy all
*#run
*#plot vin vout
.tran 1n 3u
Vin Vin 0 DC 0 SIN 0 1 1MEG
R1 Vin Vout 1k
R2 Vout 0 2k
.end
```



## Example-12 ( RC Circuit )

 

 
```
*#destroy all
*#run
*#plot vin vout
.tran 10u 16m
Vin Vin 0 DC 0 SIN 0 1 200
R1 Vin Vout 1k
CL Vout 0 1u
.end
```







# Example-13 ( RC Circuit )

 
 
```
*#destroy all
*#run
*#plot vin vout
.tran 10u 16m
Vin Vin 0 DC 0 SIN 0 1 200
R1 Vin Vout 1k
C1 Vin Vout 2u
C2 Vout 0 1u
.end
```



# Example-14 ( AC Analysis )

 

```

*#destroy all
*#run
*#plot db(vout/vin)
*#set units=degrees
*#plot ph(vout/vin)

```


```
.ac dec nd fstart fstop
```

```
.ac dec 100 1 10k
```

|     |      |      |    |   |     |   |   |     |    |   |
|-----|------|------|----|---|-----|---|---|-----|----|---|
| Vin | Vin  | 0    | DC | 0 | SIN | 0 | 1 | 200 | AC | 1 |
| R1  | Vin  | Vout | 1k |   |     |   |   |     |    |   |
| CL  | Vout | 0    | 1u |   |     |   |   |     |    |   |

```
.end
```
 
$$20 \cdot \log(0.623) = -4.11 \text{ dB}$$



We can add a phase shift of 45 degrees by using AC 1 45 in the statement.

# Important Terms ( AC)

- **Decades** : Multiplying or dividing a frequency by 10
  - Example: One decade above 23 MHz is 230 MHz.
  - Example: One decade below 1.2 kHz is 120 Hz.
- **Octaves**: Multiplying or dividing a frequency by 2.
  - Example: One octave above 23 MHz is 46 MHz.
  - Example: One octave below 1.2 kHz is 600 Hz.
  - Two octaves above 23 MHz would be 92 MHz (multiply by 4).
- **Decibels (dB) Magnitude Changes**:
  - Decreasing the magnitude response by a factor of 10 corresponds to a drop of 20 dB.
  - Increasing the magnitude by a factor of 10 corresponds to a rise of 20 dB.

# Important Terms ( AC)

## Frequency Roll-Off:


- For every increase in frequency by 10, the magnitude response decreases by 10.
- **Example** :Above 159 Hz, the response rolls off at 20 dB/decade.
- For every doubling (x2) in frequency, the magnitude response decreases by 2
- **Example** : response rolls off at 6 dB/octave above 159 Hz.

## Comparison of Roll-Off Rates

- 6 dB/octave = 20 dB/decade.
- For a roll-off rate of 40 dB/decade, every frequency increase by 10 leads to a magnitude drop by 100.
- Similarly, at 12 dB/octave, doubling the frequency results in a magnitude drop by 4.
 
# Example-15 (Pulse Statement)


0 to 1 V  
delay 6ns  
time at 1 V = 3 ns  
period = 10 ns



.tran 100p 30n


pulse vinit vfinal td tr tf pw per

|          |           |           |    |   |                         |
|----------|-----------|-----------|----|---|-------------------------|
| $V_{in}$ | $V_{in}$  | 0         | DC | 0 | pulse 0 1 6n 0 0 3n 10n |
| R1       | $V_{in}$  | $V_{out}$ | 1k |   |                         |
| C1       | $V_{out}$ | 0         | 1p |   |                         |

 

 
# Example-15 (Step Response –Positive Going)

0 to 1 V  
delay 6ns  
time at 1 V = 3 ns  
period = 10 ns




Vin Vin 0 DC 0 pulse 0 1 2n 10p

|     |      |      |    |   |                         |
|-----|------|------|----|---|-------------------------|
| Vin | Vin  | 0    | DC | 0 | pulse 0 1 6n 0 0 3n 10n |
| R1  | Vin  | Vout | 1k |   |                         |
| C1  | Vout | 0    | 1p |   |                         |

 
 
# Example-15 (Step Response –Negative Going)

0 to 1 V  
delay 6ns  
time at 1 V = 3 ns  
period = 10 ns




Vin Vin 0 DC 0 pulse -1 -2 2n 10p

.tran 100p 30n

|     |      |      |    |   |                         |
|-----|------|------|----|---|-------------------------|
| Vin | Vin  | 0    | DC | 0 | pulse 0 1 6n 0 0 3n 10n |
| R1  | Vin  | Vout | 1k |   |                         |
| C1  | Vout | 0    | 1p |   |                         |

$$t_d \approx 0.7RC$$

$$t_r \approx 2.2RC$$

 


# Example-16 (Piece-Wise Linear Source)

The piece-wise linear (PWL) source specifies arbitrary waveform shapes

```
pwl t1 v1 t2 v2 t3 v3 ... <rep>
```

```
pwl 0 0.5 3n 1 5n 1 5.5n 0 7n 0
```

 




# Example-17 (Switches)

- The switch is closed when the node voltage **controlp** is greater than the node voltage **controlm**
- Switch is modeled using the .model statement
- On Series resistance of the switch to 1k can be set


```
s1 node1 node2 controlp controlm switmod  
.model switmod sw ron=1k
```
 
```
s1 node1 node2 controlp controlm switmod
```


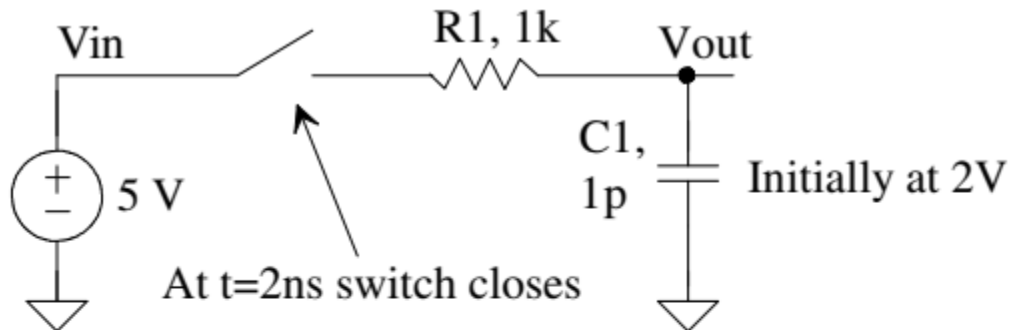
# Example-18 (Initial Condition - Capacitor)

SPICE "use initial conditions" or skip an initial operating



```
*#destroy all  
*#run  
*#plot vout
```


```
.tran 100p 8n UIC
```

```
Vclk clk 0 pulse -1 1 2n  
Vin Vin 0 DC 5  
S1 Vin Vouts clk 0 switmodel  
R1 Vouts Vout 1k  
C1 Vout 0 1p IC=2
```



```
.model switmodel sw ron=0.1
```

```
.end
```

```
.ic v(vout)=2
```

 
  
# Example-19 (Initial Condition - Inductor)



```
*#destroy all  
*#run  
*#plot vout
```

```
.tran 100p 8n UIC
```

```
Vclk clk 0 pulse -1 1 2n
```

```
Vin Vin 0 DC 5
```

```
R1 Vin Vouts1k
```

```
S1 Vouts Vout 0 clk switmodel
```

```
R2 Vout 0 1k
```


```
L1 Vout 0 10u IC=5m
```

```
.model switmodel sw ron=0.1
```

```
.end
```
 
# Example-20 (Q of an LC Tank)

$$Q = \frac{f_{center}}{BW} = \frac{f_{center}}{f_{3dBhigh} - f_{3dBlow}}$$



```
*#destroy all  
*#run  
*#plot db(vout)
```

```
.AC lin 100 400MEG 600MEG
```

```
lin Vout 0 DC 0 AC 1
```



```
R1 Vout 0 1k
```

```
L1 Vout 0 10n
```

```
C1 Vout 0 10p
```

```
.end
```

# Example-21 (Integrator Response)

  

```

*#destroy all
*#run
*#plot db(vout/vin)
*#set units=degrees
*#plot ph(vout/vin)
    
```

```

.ac dec 100 1 10k
    
```



```

Vin Vin 0 DC 1 AC 1
Rin Vin vm 1k
Cf Vout vm 1u
    
```

```

X1 Vout 0 vm Ideal_op_amp
.subckt Ideal_op_amp Vout Vp Vm
G1 Vout 0 Vm Vp 1MEG
RL Vout 0 1
.ends
.end
    
```

# Example-22 (Integrator Time Domain)

  

$$V_{out} = \frac{1}{C} \int \frac{V_{in}}{R} \cdot dt$$

$$V_{out}(t) = \frac{V_{in}}{RC} = \frac{1}{1 \text{ ms}}$$

```
*#destroy all
*#run
*#plot vout vin
```

```
.tran 10u 10m
.ic v(vout)=0
```

```
Vin Vin 0 DC 1
+ pulse -1 1 0 1u 1u 2m 4m
Rin Vin vm 1k
Cf Vout vm 1u
```

```
X1 Vout 0 vm Ideal_op_amp
.subckt Ideal_op_amp Vout Vp Vm
G1 Vout 0 Vm Vp 1MEG
RL Vout 0 1
.ends
.end
```

# Summary

- **Key for Circuit Validation:** SPICE simulates circuit behavior, reducing errors before fabrication
- **Accurate Modeling:** Provides realistic predictions of performance and reliability
- **Enables Optimization:** Guides efficient design adjustments for power, speed, and area
- **Flexible Convergence:** Adjustable settings aid simulations of complex VLSI circuits.



**Chip design bole toh potato chip  
samhje kya?**

**VLSI Engineer Hai main**

**Thank you !  
Happy Learning**