

# CMOS Circuit Design Styles

## PTL and TG

**Pravin Zode**

# Outline

- Merits of Static CMOS Circuits
- Bubble Pushing and CMOS circuits
- Ratioed Circuits
- Cascode Voltage Switch Logic (CVSL)
- Pass Transistor Logic (PTL)
- Transmission Gate Circuits

# Introduction

- Static CMOS circuits are used for the vast majority of logic gates in integrated circuits as they have
  - Good noise margins,
  - Fast and low power
  - Insensitive to device variations
  - Easy to design
  - Widely supported by CAD tools
  - Readily available in standard cell libraries


# Static CMOS

- Designers accustomed to AND and OR functions must learn to think in terms of NAND and NOR to take advantage of static CMOS
- In manual circuit design, this is often done through bubble pushing
- Compound gates are particularly useful to perform complex functions with relatively low logical efforts
- Using smaller pMOS transistors can reduce power, area, and delay
 
# Bubble Pushing

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$


$$\overline{A + B} = \bar{A} \cdot \bar{B}$$




- CMOS stages are inherently inverting, so AND and OR functions must be built from NAND and NOR gates
- NAND gate is equivalent to an OR of inverted inputs
- NOR gate is equivalent to an AND of inverted inputs
 
# Example


Design a circuit to compute  $F = AB + CD$  using NANDs and NORs




(a)

 

(b)

 

(c)


 


(d)

# AOI Gates

Unit Inverter

$$Y = \overline{A}$$

  


$$g_A = 3/3$$

$$p = 3/3$$

AOI21

$$Y = \overline{A \cdot B + C}$$

 

$$g_A = 6/3$$



$$g_B = 6/3$$

$$g_C = 5/3$$

$$p = 7/3$$

AOI22

$$Y = \overline{A \cdot B + C \cdot D}$$

  

$$g_A = 6/3$$

$$g_B = 6/3$$



$$g_C = 6/3$$

$$g_D = 6/3$$

$$p = 12/3$$

Complex AOI
  
$$Y = \overline{A \cdot (B + C) + D \cdot E}$$



$$g_A = 5/3$$

$$g_B = 8/3$$

$$g_C = 8/3$$


$$g_D = 8/3$$

$$g_E = 8/3$$

$$p = 16/3$$

 
# Introduction

- What makes a circuit fast?
  - $I = C \, dV/dt \rightarrow t_{pd} \propto (C/I) \Delta V$
  - low capacitance
  - high current
  - small swing
- Logical effort is proportional to  $C/I$
- pMOS are the enemy!
  - High capacitance for a given current
- Can we take the pMOS capacitance off the input?
- Various circuit families try to do this...






# Ratioed Logic

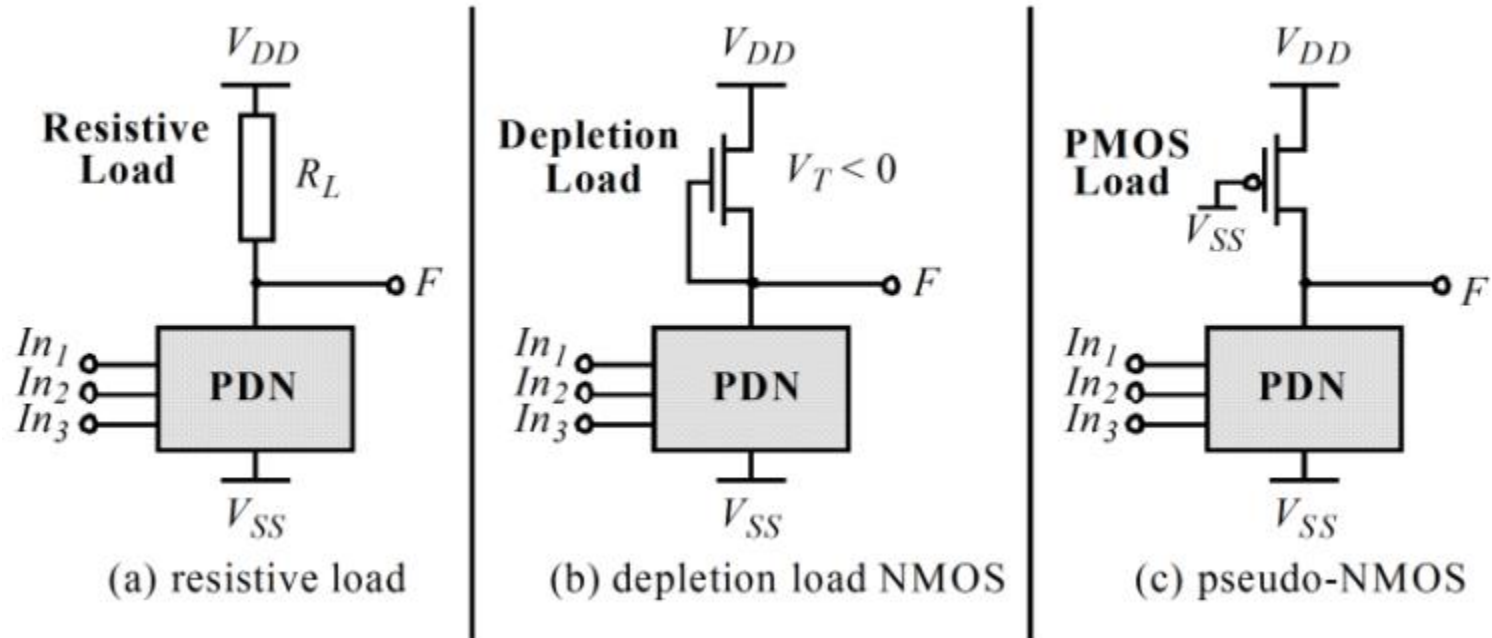


Goal : to reduce the number of devices over complementary CMOS

# Ratioed Logic

 


- **N transistors + Load**
- $V_{OH} = V_{DD}$
- $V_{OL} = \frac{R_{PDN}}{R_{PDN} + R_L} V_{DD}$
- **Assymetrical response ( $t_r > t_f$ )**
- **Static power consumption**
- $t_{pLH} = 0.69 R_L C_L$

# Active Loads

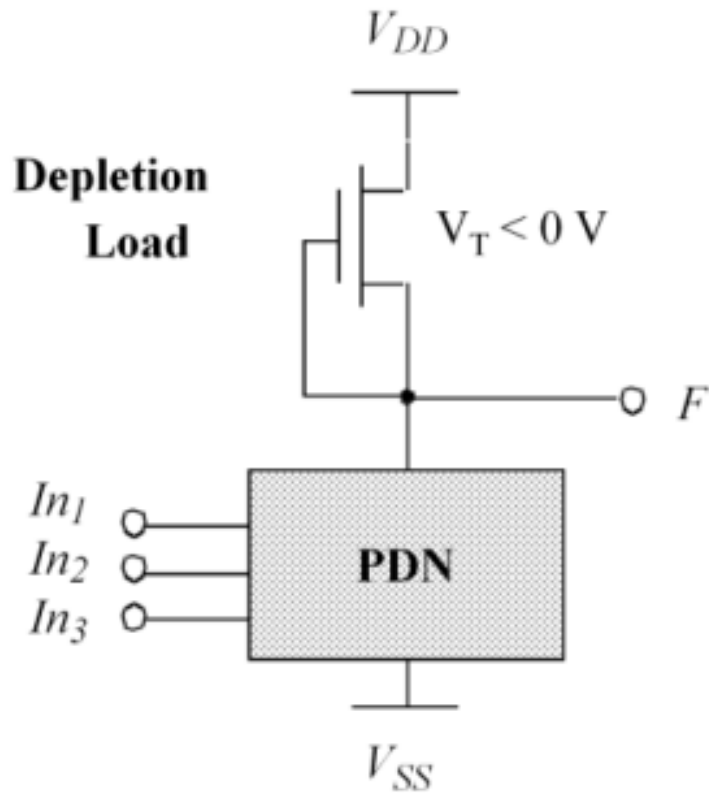


depletion load NMOS

 

pseudo-NMOS


# Pseudo NMOS NOR Gate

 



Smaller Area and load but Static Power Dissipation
 
# Pseudo-nMOS Power

- Pseudo-nMOS draws power whenever  $Y = 0$ 
  - Called static power  $P = I_{DD} V_{DD}$
  - A few mA / gate \* 1M gates would be a problem
- Use pseudo-nMOS sparingly for wide NORs
- Turn off pMOS when not in use





# Ganged CMOS

  


$$\begin{aligned} g_u &= 1 \\ g_d &= 2/3 \\ g_{avg} &= 5/6 \end{aligned}$$

A	B	N1	P1	N2	P2	Y
0	0	OFF	ON	OFF	ON	1
0	1	OFF	ON	ON	OFF	~ 0
1	0	ON	OFF	OFF	ON	~ 0
1	1	ON	OFF	ON	OFF	0

# Cascode Voltage Switch Logic

  

# CVSL – XOR Gate 4 Input

 

4-Input CVSL XOR Gate




# Summary CVSL




- A differential CMOS logic style that uses a dual-rail structure to provide both true and complementary outputs.
- High speed, reduced power dissipation, and good noise immunity due to its differential nature.
- Increased transistor count and design complexity compared to standard CMOS.
- Suitable for high-performance VLSI circuits, especially in noise-sensitive and high-speed applications

# Pass Transistor Logic

# NMOS Switch as Pass Gate

 


# PMOS Switch as Pass Gate

   


AND gate using pass transistor logic


# Pass Transistor Gate

 


AND Gate

 

NOR Gate



 


OR Gate

 

NAND Gate

# Pass Transistor Gate

  
 


$$\text{Implement } F = \frac{(A + B) \cdot C}{(\bar{A} + \bar{B}) + \bar{C}}$$

$$\bar{A} \cdot \bar{B} + \bar{C}$$

 
 
# Problem with PTL

Pass Transistor Logic gates cannot be cascaded by connecting the output of a pass gate to the gate input of another pass transistor




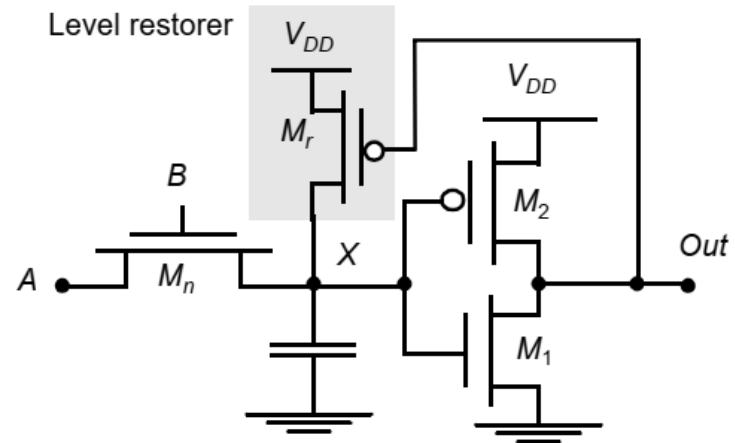
 
# Level Restorer with PTL

A level restorer is typically implemented using PMOS transistors. It works by pulling the degraded high signal back to the full  $V_{DD}$ .






   
# Complimentary/Differential Pass Transistor Logic



AND/NAND


 


OR/NOR

 


XOR/NXOR

# NAND Gate ( 4 Input CPL)

 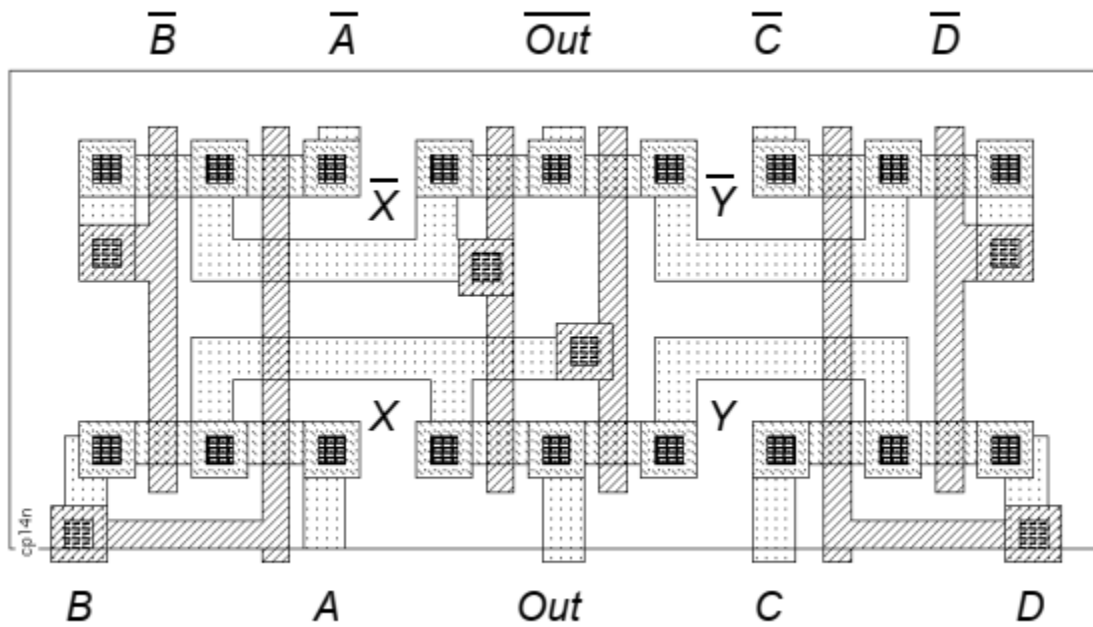

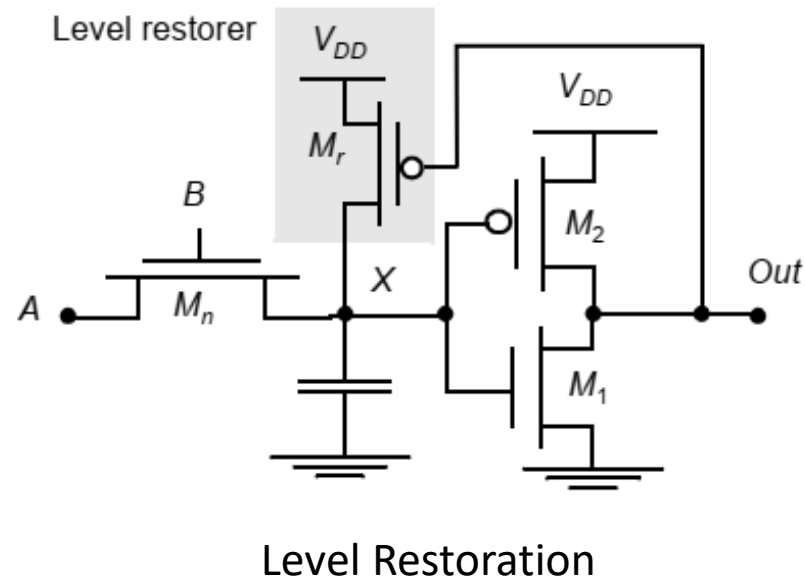
# Robust and Efficient Pass-Transistor Design

- Solution for robust and efficient PTL
  - Level Restoration
  - Multiple Threshold Transistors
  - Transmission Gate Logic



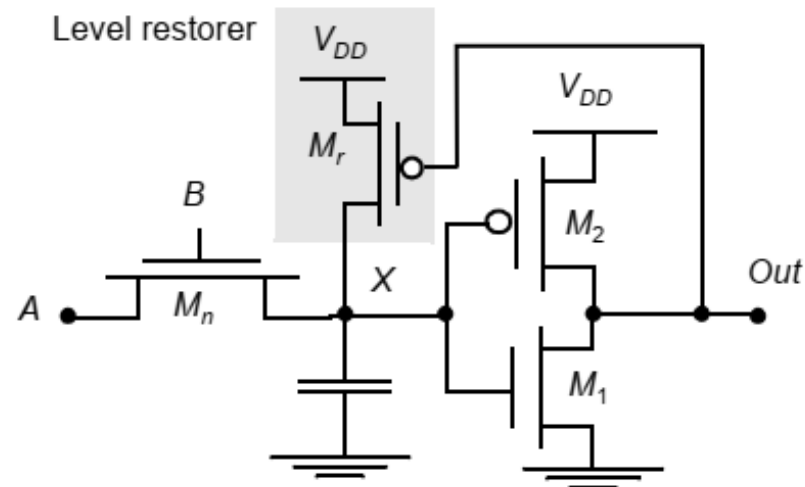
# Robust and Efficient Pass-Transistor Design

- Solution for robust and efficient PTL
  - Level Restoration
  - Multiple Threshold Transistors
  - Transmission Gate Logic




Level Restoration


# Pass Transistor Logic Design

 


Controlled Inverter

 


Inverter with Tristate

 

Inverter with Tristate

 



XOR Gate

 

XNOR Gate

  
# PTL Based Mux

$$F = \bar{A} \bar{B} I_0 + \bar{A} B I_1 + A \bar{B} I_2 + A B I_3$$


 
# Transmission Gate Logic

- CMOS transmission gates overcome the weak logic levels of single-pass transistors.
- Use two complementary transistors (nMOS + pMOS) to ensure robust logic levels.



$g = 0, gb = 1$

$a \rightarrow b$

$g = 1, gb = 0$

$a \rightarrow b$

Input




Output

$g = 1, gb = 0$


$0 \rightarrow \text{strong } 0$

$g = 1, gb = 0$

$1 \rightarrow \text{strong } 1$

   


# Mux using Transmission Gate Logic

 

 **Transistor count: 14**

- 4 transistors per NAND gate,
- 2 for the inverter





**Transistor count: 6**

- 4 for transmission gates
- 2 for inverter



# XOR Gate using Transmission Gate Logic

  

## Transistor Counts :

- 12 transistors for conventional CMOS
- 6 or 8 Transistors for TG



**Thank you !**

**Happy Learning**